

	GOVT. MODEL ENGINEERING COLLEGE, THRIKKAKARA (Managed by IHRD, A Govt. of Kerala Undertaking) DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING			
B.TECH. DEGREE FIRST SEMESTER ELECTRONICS AND BIOMEDICAL ENGINEERING SECOND INTERNAL EXAMINATION – MARCH 2021			Academic Year: 2020-21	
`SLOT :D	Course Code: EST 130	Course Title: Basics of electrical and electronics engineering		
Duration: 45 min	Max. Marks: 25	Faculty Handling the Course: Vidya K ,Asha Deepthi ,Thakku Peter		
<i>Course Outcomes: At the end of the course the students will be able to</i>				
<i>EST 130.1</i>	<i>Understand the basic concepts of circuit parameters/components, Understand basic laws for the analysis of electric circuits</i>			
<i>EST 130.2</i>	<i>Understand basic laws for the analysis of magnetic circuits</i>			
<i>EST 130.3</i>	<i>Analyze single phase systems, Analyze three phase ac systems for balanced and unbalanced loading.</i>			
(Answer All Questions)			CO	Marks
1	Compare electric and magnetic circuits by their similarities and dissimilarities.		EST130.2	5
2	Derive the peak factor and form factor of half wave rectified sinusoidal waveform.		EST130.2	5
3	Explain in detail the theory of sinusoidal AC response of RLC series circuit with neat circuit and phasor diagrams.		EST130.3	5
4	A metal ring of mean diameter of 80 cm is made out of two semi-circular pieces of cast iron and cast steel separated at junctions by pieces of copper each of 1 mm thickness. If the ring is uniformly wound with 1000 turns, calculate the value of current required to produce a flux density of 0.85 wb/m ² in the ring. Given that relative permeability of cast iron as 200, that of cast steel is 1200 and for copper, $\mu_r = 1$.		EST130.2	5
5	A balanced three phase load consists of three coils each having resistance of 4 Ω and inductance 0.02H. It is connected to a 415V, 50Hz, 3-phase ac supply. Determine the phase voltage, phase current, power factor and active power when the loads are connected in (i) star (ii) delta.		EST130.3	5